

# Measuring light with an Arduino

Posted on [November 3, 2013](#)

The easiest way to measure light with an Arduino is with an LDR.

LDR's (Light dependend resistors) have a low resistance in bright light and a high resistance in the darkness.

If you would use the LDR as the lower part of a voltage divider, then in darkness there would be a high voltage over the LDR, while in bright light, there would be a low voltage over that resistor.

Ofcourse if you would use it as the upper part of a voltage divider, it would be the reverse: low voltage in the darkness, high voltage in bright light

Doing that on an Arduino Analog port, would give a reading between 0 and 1024, which ofcourse are really non-descriptive numbers.

What you would want is an output in Lux or Lumen

That is possible but mind you that LDR's are not really accurate for precise readings.

There is a somewhat rough formula that relates the resistance of an LDR to the light in Lux. That is:

$$R_{ldr} = 500 / \text{Lux}, \text{ or}$$

$$\text{Lux} = 500 / R_{ldr} \text{ (in kOhm)}$$

as  $R_{ldr}$  is related to the voltage measured over it, reading the Voltage over it, can be used to calculate the  $R_{ldr}$  and thus the Lux level

If the LDR is the lower part of a 5 Volt Voltage divider and a 10kOhm resistor the upper part, the Voltage will be:

$$V_{out} = (5 / (10 + R_{ldr})) * R_{ldr}$$

$$V_{out} = 5 * R_{ldr} / (10 + R_{ldr}) \text{ (remember: multiplication before division)}$$

as we do not measure a voltage, but a value between 0 and 1024, every step can be defined by  $5/1024 = 0.0048828125$ .

$$\Rightarrow V_{out} = \text{Analogreading} * 0.0048828125$$

$$\text{as } R_{ldr} = (10 * V_{out}) / (5 - V_{out}) \text{ (remember } R_{ldr} \text{ is expressed in kOhm)}$$


$$\Rightarrow \text{Lux} = (500 * (5 - V_{out})) / (10 * V_{out})$$

$$\Rightarrow \text{Lux} = (2500 - 500 * V_{out}) / (10 * V_{out})$$

$$\Rightarrow \text{Lux} = (2500 / V_{out} - 500) / 10$$

$$\Rightarrow \text{Lux} = (2500 / ((\text{AnalogRead} * 0.0048828125) - 500)) / 10$$

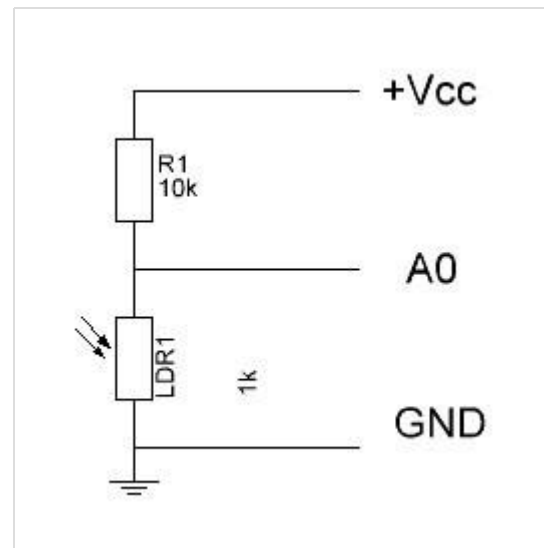Anyway, in an arduino program that will look like:





```
//Lux
double Light (int RawADC0){
double Vout=RawADC0*0.0048828125;
//int lux=500/(10*((5-Vout)/Vout));//use this equation if the LDR is in the upper part of
the divider
int lux=(2500/Vout-500)/10;
return lux;
}
void setup() {
Serial.begin(115200);
}
void loop() {
Serial.println(int(Light(analogRead(0))));
delay(1000);
}
```

Anyway, as said, an LDR is not the most accurate to measure light intensity. A photodiode would be better

Full work out of the Formula, for those interested (remember, this expresses  $R_{ldr}$  in kiloOhm and is for a 10kOhm reference resistor:

$$V_{out} = (5R_{ldr}) / (R_{ldr} + 10)$$

$$5R_{ldr} = V_{out}(R_{ldr} + 10) \quad // \text{multiplied both sides with } (R_{ldr} + 10) \text{ and switch left and right}$$

$$5R_{ldr} = V_{out} * R_{ldr} + 10V_{out} \quad // \text{executed the right side multiplication}$$

$$5R_{ldr} + (-V_{out} * R_{ldr}) = (V_{out} * R_{ldr} + 10V_{out}) + (-V_{out} * R_{ldr}) \quad // \text{added equal value } (-V_{out} * R_{ldr}) \text{ to both sides}$$

$$5R_{ldr} + (-V_{out} * R_{ldr}) = V_{out} * R_{ldr} + 10V_{out} - V_{out} * R_{ldr} \quad // \text{work out right side additions and subtractions}$$

$$5R_{ldr} - V_{out} * R_{ldr} = V_{out} * R_{ldr} + 10V_{out} - V_{out} * R_{ldr} \quad // \text{work out left side additions and subtractions}$$

$$5R_{ldr} - V_{out} * R_{ldr} = V_{out} * R_{ldr} - V_{out} * R_{ldr} + 10V_{out} \quad // \text{ditto}$$

$$5R_{ldr} - V_{out} * R_{ldr} = 10V_{out} \quad // \text{ditto}$$

$$R_{ldr}(5 - V_{out}) = 10V_{out} \quad // \text{expressed left side as multiplication of } R_{ldr}$$

$$R_{ldr} = 10V_{out} / (5 - V_{out}) \quad // \text{divided both sides by equal value } (5 - V_{out})$$

For a reference resistor other than 10k the solution is as follows

$$R_{ldr} = (R_{ref} * V_{out}) / (5 - V_{out})$$

Also.. remember that though we expressed the value of  $R_{ldr}$  as a function of  $V_{out}$ , ofcourse the value does not depend on  $V_{out}$ , it is the other way around, but it is necessary to inject the function of  $V_{out}$  into the Lux formula

#### SHARE THIS:



Be the first to like this.



---

## RELATED

[Analog sensors on a Raspberry PI](#)

[Chosing a pull down resistor for an LDR: Axel Benz formula](#)

[Using the Attiny's Reset Pin without setting Fuse Bits In "Attiny"](#)

This entry was posted in [Uncategorized](#) and tagged [arduino](#), [LDR](#), [Lux](#) by [Arduino](#). Bookmark the [permalink](#) [<https://arduino diy.wordpress.com/2013/11/03/measuring-light-with-an-arduino/>] .

5 THOUGHTS ON "MEASURING LIGHT WITH AN ARDUINO"



**rinaerwiza**

on [December 22, 2013 at 8:04 am](#) said:

whether a reference book on the formula

=>  $Lux = (500 * (5 - V_{out})) / (10 * V_{out})$

and where it comes from 500



**Arduino**

on [December 22, 2013 at 12:36 pm](#) said:

Found it somewhere on internet but as i am travelling right now it is a bit hard to search for the link



**Sonicon Lab**

on [January 4, 2014 at 6:29 pm](#) said:

I tested the above code with this sensor (<http://www.fezhydra.com/GHI-Light-Sensor-3-Pin-eblock/dp/B00614OY6K>), an Arduino Uno, and an Android application as a reference to check the values (<https://play.google.com/store/apps/details?id=com.bti.lightMeter&hl=en>).

However I get different indications – especially when there is a lot of brightness.

Is there any tip on how to calibrate it correctly?

[+ Follow](#)



Arduino

on [January 8, 2014 at 5:34 am](#) said:

I am not sure. I used the formula as is. Will look into it



Arduino

on [January 14, 2014 at 2:41 pm](#) said:

Sonicon, The formula is a rough approach. If you want precise readings you best make a look up table in which you have lux value for a specific reading by your Arduino, or for a specific resistance of the LDR.

For that table of course you need a Luxmeter, but if you know a photographer with a Lightmeter.... these will indicate the amount in LUX

[+ Follow](#)